

# Boolean Logic Worksheet

1. Complete the following truth table.

A	B	AND	OR	XOR	NOT A	NAND	NOR
0	0						
0	1						
1	0						
1	1						

2. Complete the following truth table for the Boolean expression

**A AND (B OR A)**

A	B	(B OR A)	A AND (B OR A)
0	0		
0	1		
1	0		
1	1		

3. Complete the following truth table for the Boolean expression

**NOT A AND B XOR A**

A	B	NOT A	NOT A AND B	NOT A AND B XOR A
0	0			
0	1			
1	0			
1	1			

4. Create a truth table for the Boolean expression

**A NAND (B NOR A)**

A	B	(B NOR A)	A NAND (B NOR A)
0	0		
0	1		
1	0		
1	1		

5. Complete the following truth table for the Boolean expression


$$(A \text{ XOR } B) \text{ OR } (A \text{ NAND } C)$$

A	B	C	(A XOR B)	(A NAND C)	OR
0	0	0			
0	1	0			
1	0	0			
1	1	0			
0	0	1			
0	1	1			
1	0	1			
1	1	1			




6. Create a logic diagram for the following Boolean expression.

$$(A \text{ AND } B) \text{ OR } B$$

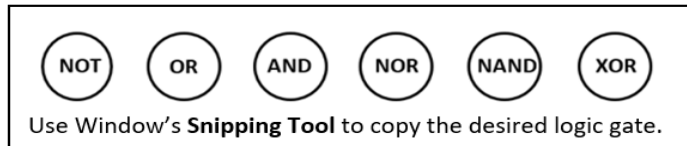

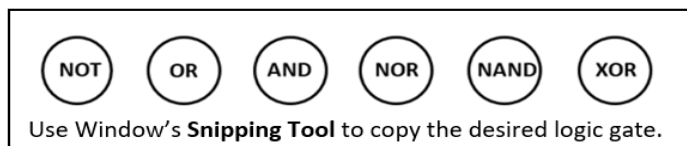7. Create a logic diagram for the following Boolean expression.

$$(A \text{ OR NOT } B) \text{ OR } (A \text{ NAND } B)$$



8. Create a logic diagram for the following Boolean expression.

$$A \text{ OR } (A \text{ XOR } B)$$



9. Create a logic diagram for the following Boolean expression.

A XOR B OR B AND C